

# Fast analytical techniques for electrical and electronic circuits

---

**Vatché Vorpérian**

Jet Propulsion Laboratory  
California Institute of Technology



PUBLISHED BY THE PRESS SYNDICATE OF THE UNIVERSITY OF CAMBRIDGE  
The Pitt Building, Trumpington Street, Cambridge, United Kingdom

CAMBRIDGE UNIVERSITY PRESS  
The Edinburgh Building, Cambridge CB2 2RU, UK,  
40 West 20th Street, New York, NY 10011-4211, USA  
477 Williamstown Road, Port Melbourne VIC 3207, Australia  
Ruiz de Alarcón 13, 28014 Madrid, Spain  
Dock House, The Waterfront, Cape Town 8001, South Africa  
<http://www.cambridge.org>

© Cambridge University Press 2002

This book is in copyright. Subject to statutory exception  
and to the provisions of relevant collective licensing agreements,  
no reproduction of any part may take place without  
the written permission of Cambridge University Press.

First published 2002

Printed in the United Kingdom at the University Press, Cambridge

*Typeface* Times 10.5/14pt *System* Poltype® [vN]

*A catalogue record for this book is available from the British Library*

ISBN 0 521 62442 8 hardback

# Contents

<i>Preface</i>	xi
----------------	----

---

<b>1</b>	<b>Introduction</b>	1
1.1	Fast analytical methods	1
1.2	Input impedance of a bridge circuit	2
1.3	Input impedance of a bridge circuit with a dependent source	4
1.4	Input impedance of a reactive bridge circuit with a dependent source	8
1.5	Review	11
	Problems	11
	References	14

---

<b>2</b>	<b>Transfer functions</b>	15
2.1	Definition of a transfer function	15
2.2	The six types of transfer functions of an electrical circuit	17
2.3	Determination of the poles of a network	19
2.4	Determination of the zeros of a transfer function	24
2.5	The complete response, stability and transfer functions	34
2.6	Magnitude and phase response	41
2.7	First-order transfer functions	43
2.8	Second-order transfer functions	48
2.9	Review	52
	Problems	53

---

<b>3</b>	<b>The extra element theorem</b>	61
3.1	Introduction	61
3.2	Null double injection	62

---

3.3	The EET for impedance elements	74
3.4	The EET for dependent sources	88
3.5	Review	98
	Problems	99
	References	106

---

## 4 The $N$ -extra element theorem 107

---

4.1	Introduction	107
4.2	The 2-EET for impedance elements	108
4.3	The 2-EET for dependent sources	130
4.4	The NEET	137
4.5	A proof of the NEET	147
4.6	Review	153
	Problems	154
	References	162

---

## 5 Electronic negative feedback 163

---

5.1	Introduction	163
5.2	The EET for dependent sources and formulation of electronic feedback	164
	5.2.1 Gain analysis	164
	5.2.2 Driving-point analysis	170
	5.2.3 Loop gain	175
5.3	Does this <i>circuit</i> have feedback or not? This is <i>not</i> the question	179
5.4	Gain analysis of feedback amplifiers	180
5.5	Driving-point analysis of feedback amplifiers	195
	5.5.1 Input <i>impedance</i> for current mixing	196
	5.5.2 Output <i>impedance</i> for voltage sensing	200
	5.5.3 Input <i>admittance</i> for voltage mixing	204
	5.5.4 Output <i>admittance</i> for current sensing	209
5.6	Loop gain: a more detailed look	213
5.7	Stability	218
5.8	Phase and gain margins	226
5.9	Review	233
	Problems	234
	References	251

<b>6</b>	<b>High-frequency and microwave circuits</b>	252
6.1	Introduction	252
6.2	Cascode MOS amplifier	252
6.3	Fifth-order Chebyshev low-pass filter	261
6.4	MESFET amplifier	265
6.5	Review	310
	Problems	311
	References	316
<b>7</b>	<b>Passive filters</b>	317
7.1	Introduction	317
7.2	$RC$ filters with gain	317
7.3	Lattice filters	327
7.4	Resonant filters	335
	7.4.1 Parallel resonant filters	336
	7.4.2 Tapped parallel resonant filter	339
	7.4.3 The three-winding transformer	344
7.5	Infinite scaling networks	349
	7.5.1 Infinite grid	349
	7.5.2 Infinite scaling networks	351
	7.5.3 A generalized linear element and a unified $R$ , $L$ and $C$ model	356
7.6	Review	358
	Problems	358
	References	364
<b>8</b>	<b>PWM switching dc-to-dc converters</b>	365
8.1	Introduction	365
8.2	Basic characteristics of dc-to-dc converters	366
8.3	The buck converter	370
8.4	The boost converter	386
8.5	The buck-boost converter	392
8.6	The Cuk converter	397
8.7	The PWM switch and its invariant terminal characteristics	400

8.8	Average large-signal and small-signal equivalent circuit models of the PWM switch	402
8.9	The PWM switch in other converter topologies	411
8.10	The effect of parasitic elements on the model of the PWM switch	426
8.11	Feedback control of dc-to-dc converters	432
	8.11.1 Single-loop voltage feedback control	433
	8.11.2 Current feedback control	440
	8.11.3 Voltage feedback control with peak current control	453
8.12	Review	460
	Problems	461
	References	470
	<i>Index</i>	472

# 1 Introduction

## The joys of network analysis

### 1.1 Fast analytical methods

The universally adopted method of teaching network theory is the formal and systematic method of nodal or loop analysis. Although the matrix algebra of formal network analysis is ideal for obtaining *numerical* answers by a computer, it fails hopelessly for obtaining *analytical* answers which provide physical insight into the operation of the circuit. It is not hard to see that, when numerical values of circuit components are not given, inverting a  $3 \times 3$ , or higher-order, matrix with symbolic entries can be very time consuming. This is only part of the problem of matrix analysis because even if one were to survive the algebra of inverting a matrix symbolically, the answer could be an unintelligible and lengthy symbolic expression. It is important to realize that an analytical answer is not merely a symbolic expression, but an expression in which various circuit elements are grouped together in one or more of the following ways:

- (a) series and parallel combinations of resistances

$$\text{Example: } R_1 + R_2 \parallel (R_3 + R_4)$$

- (b) ratios of resistances, time constants and gains

$$\text{Example: } 1 + \frac{R}{R_3 \parallel R_4}, 1 + \frac{g_m R_L}{A_o}, A_m \left( 1 + \frac{\tau_1}{\tau_2} \right)$$

- (c) polynomials in the frequency variable,  $s$ , with a unity leading term and coefficients in terms of sums and products of time constants

$$\text{Example: } 1 + s(\tau_1 + \tau_2) + s^2\tau_1\tau_3$$

Such analytical expressions have been called low-entropy expressions by R. D. Middlebrook<sup>1</sup> because they reveal useful and *recognizable* information (low noise or entropy) about the performance of the circuit. Another extremely important advantage of low-entropy expressions is that they can be easily approximated into simpler expressions which are useful for design purposes. For instance, a series-parallel combination of resistances, as in (a), can be simplified by ignoring the smaller of two resistances in a series combination and the larger of two resistances

in a parallel combination. When ratios are used as in (b), they can be simplified depending on their relative magnitude to unity. Depending on the relative magnitude of time constants, frequency response characteristics as in (c) can be simplified and either factored into two real roots, with simple analytical expressions, or remain as a complex quadratic factor.

In light of the above, the aim of fast analytical techniques can be stated as follows: fast derivation of low-entropy analytical expressions for electrical circuits. The following examples illustrate the power of this new approach to circuit analysis.

### 1.2 Input impedance of a bridge circuit

We will determine the input resistance,  $R_{in}$ , of the bridge circuit<sup>2</sup> in Fig.1.1 in a few simple steps using the extra element theorem (EET). The EET<sup>3</sup> and its extension, the  $N$ -extra element theorem<sup>4</sup> (NEET), are the main basic tools of fast network analysis discussed in this book. Both of these theorems will be introduced, derived and stated in their general form in later chapters, but since the EET for an impedance function is so trivial, we will use it now to obtain an early glimpse of what lies ahead.

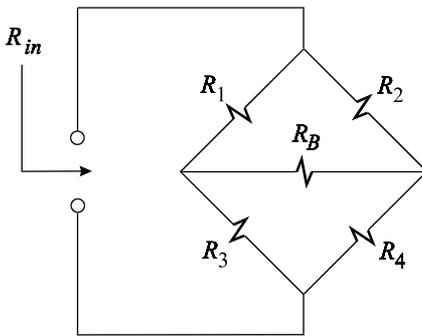


Figure 1.1

We see in Fig. 1.1 that if any one of the resistors of the bridge is zero or infinite, we can write  $R_{in}$  immediately by inspection. For instance, if we designate  $R_B$  as the extra element and let  $R_B \rightarrow \infty$ , as shown in Fig. 1.2a, we can immediately write:

$$R_{in} |_{R_B \rightarrow \infty} = (R_1 + R_3) \parallel (R_2 + R_4) \tag{1.1}$$

The EET now requires us to perform two additional calculations as shown in Figs. 1.2b and c. We denote the port across which the extra element is connected by ( $B$ ).

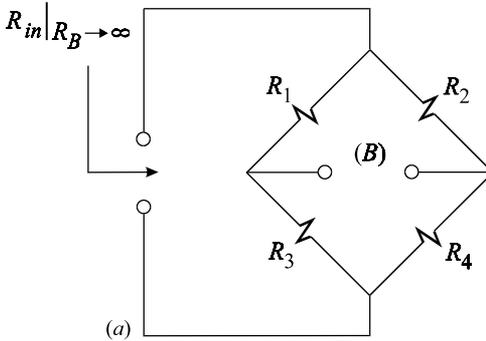


Figure 1.2

In Fig. 1.2b, we determine the resistance looking into the network from port  $(B)$  with the *input port short* and obtain by inspection:

$$\mathcal{R}^{(B)} = R_1 \parallel R_3 + R_2 \parallel R_4 \quad (1.2)$$

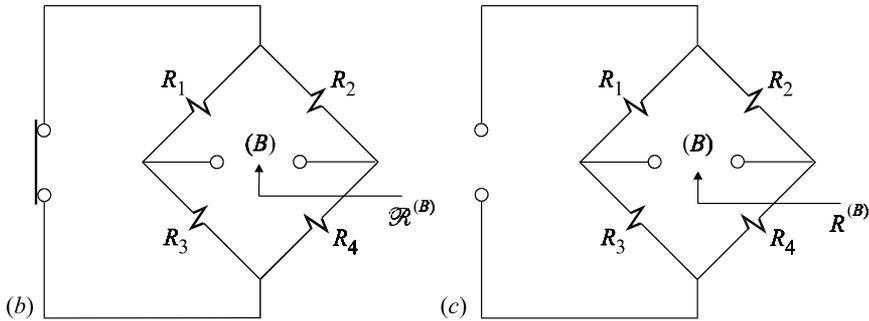


Figure 1.2 (cont.)

In Fig. 1.2c, we determine the resistance looking into the network from port  $(B)$  with the *input port open* and obtain by inspection:

$$R^{(B)} = (R_1 + R_2) \parallel (R_3 + R_4) \quad (1.3)$$

We now assemble these three separate and independent calculations to obtain the input resistance  $R_{in}$  in Fig. 1.1 using the following formula given by the EET:

$$R_{in} = R_{in} |_{R_B \rightarrow \infty} \frac{1 + \frac{\mathcal{R}^{(B)}}{R_B}}{1 + \frac{R^{(B)}}{R_B}} \quad (1.4)$$

Upon substituting Eqs. (1.1), (1.2) and (1.3) in (1.4):

$$R_{in} = (R_1 + R_3) \parallel (R_2 + R_4) \frac{1 + \frac{R_1 \parallel R_3 + R_2 \parallel R_4}{R_B}}{1 + \frac{(R_1 + R_2) \parallel (R_3 + R_4)}{R_B}} \quad (1.5)$$

Equation (1.5) is a low-entropy result because in it  $R_{in}$  is expressed in terms of series and parallel combinations of resistances and ratios of such resistances added to unity. Such an expression, for a given set of typical element values, can be easily approximated using rules of series and parallel combinations wherever applicable. In this expression, we can also see the contribution of the bridge resistance,  $R_B$ , to the input resistance,  $R_{in}$ , directly.

We can also appreciate two important advantages of the method of EET used in deriving  $R_{in}$  above. First, since the method of EET requires far less algebra than nodal analysis, it is considerably faster and simpler. Second, since the EET requires three separate and *independent* calculations, any *error in the analysis does not spread* and remains confined to a portion of the final answer. In a sense, this kind of analysis yields modular answers – if there is anything wrong with a particular module, it can be replaced without affecting the entire answer. This not only makes the analysis faster, but also the debugging of the analysis faster as well.

### 1.3 Input impedance of a bridge circuit with a dependent source

In this section we consider the effect of a dependent current source,<sup>2,5</sup>  $g_m v_1$ , in Fig. 1.3, on the input resistance  $R_{in}$ . This circuit is borrowed from a well-known

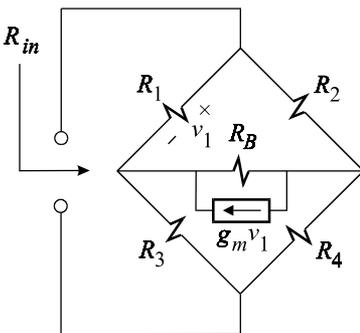


Figure 1.3

textbook by L. O. Chua and Pen-Min Lin<sup>5</sup> in which the authors determine the contribution of the transconductance,  $g_m$ , to the input resistance,  $R_{in}$ , using the

parameter-extraction method. Because of the considerable amount of matrix algebra required by the parameter-extraction method, which would become prohibitively complex if all elements were in symbolic form, Chua and Lin have assigned numerical values ( $R_1 = 1\Omega$ ,  $R_2 = 0.2\Omega$ ,  $R_3 = 0.5\Omega$ ,  $R_4 = 10\Omega$  and  $R_B = 0.1\Omega$ ) to all the resistors and determined:

$$R_{in} = \frac{96.3 + 5.1g_m}{137.7 + 10.5g_m} \Omega \quad (1.6)$$

We will now show how to determine  $R_{in}$  in three simple steps by applying the EET to the dependent current source  $g_m v_1$ . To demonstrate the superior power of this method of analysis, we will keep all circuit elements in symbolic form.

In Fig. 1.3, we designate the dependent current source as the extra element and set it to zero by letting  $g_m = 0$ . This reduces the circuit to the bridge circuit in Section 1.2, as shown in Fig. 1.4a. Hence, we have from Eq. (1.5):

$$R_{in}|_{g_m \rightarrow 0} = (R_1 + R_3) \parallel (R_2 + R_4) \frac{1 + \frac{R_1 \parallel R_3 + R_2 \parallel R_4}{R_B}}{1 + \frac{(R_1 + R_2) \parallel (R_3 + R_4)}{R_B}} \quad (1.7)$$

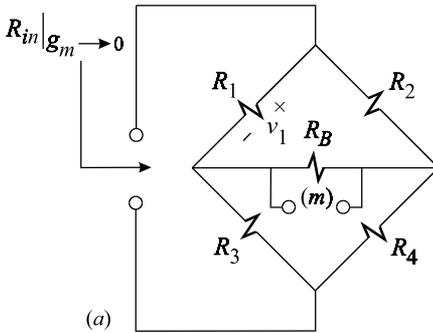


Figure 1.4

The EET now requires us to perform two additional calculations as shown in Figs. 1.4b and c in which the dependent current source is replaced with an independent one,  $i_m$ , pointing in the opposite direction. In Fig. 1.4b we determine the transresistance,  $v_1/i_m$ , which is the *inverse* of the transconductance gain  $g_m$  of the dependent source, with the input port short. Inspecting Fig. 1.4b, we see that  $R_1 \parallel R_3$  and  $R_2 \parallel R_4$  form a voltage divider connected across an equivalent Thevenin voltage source,  $i_m R_B$ , in series with a Thevenin resistance,  $R_B$ , so that we have:

$$\frac{v_1}{i_m R_B} = \frac{R_1 \parallel R_3}{R_B + R_2 \parallel R_4 + R_1 \parallel R_3} \quad (1.8)$$

It follows that the inverse gain, with the input port short, is given by:

$$\bar{\mathcal{G}}^{(m)} = \frac{v_1}{i_m} \Big|_{(in) \rightarrow short} = \frac{R_1 \parallel R_3}{R_B + R_2 \parallel R_4 + R_1 \parallel R_3} R_B \quad (1.9)$$

Similarly, we can determine in Fig. 1.4c that the inverse gain, with the input port open, is given by:

$$\bar{G}^{(m)} = \frac{v_1}{i_m} \Big|_{(in) \rightarrow open} = \frac{R_B \parallel (R_3 + R_4)}{R_1 + R_2 + R_B \parallel (R_3 + R_4)} R_1 \quad (1.10)$$

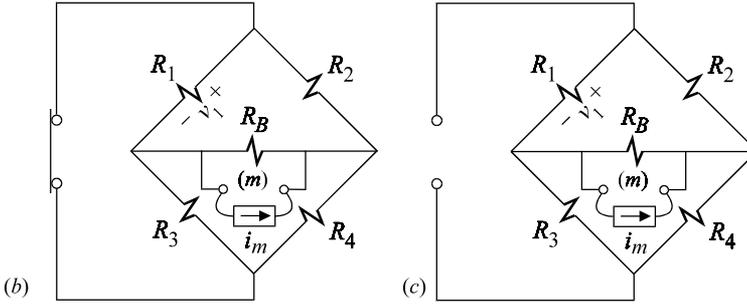


Figure 1.4 (cont.)

We can now assemble the final answer using the three separate calculations in Eqs. (1.7), (1.9) and (1.10) according to the following formula given by the EET:

$$R_{in} = R_{in} \Big|_{g_m \rightarrow 0} \frac{1 + g_m \bar{\mathcal{G}}^{(m)}}{1 + g_m \bar{G}^{(m)}} \quad (1.11)$$

Upon substituting, we get:

$$R_{in} = (R_1 + R_3) \parallel (R_2 + R_4) \frac{1 + \frac{R_1 \parallel R_3 + R_2 \parallel R_4}{R_B}}{1 + \frac{(R_1 + R_2) \parallel (R_3 + R_4)}{R_B}} \quad (1.12)$$

$$\times \frac{1 + \frac{g_m R_B}{1 + (R_B + R_2 \parallel R_4)/R_1 \parallel R_3}}{1 + \frac{g_m R_1}{1 + (R_1 + R_2)/R_B \parallel (R_3 + R_4)}}$$

Hence, by doing far less algebra than that required by the parameter-extraction

method, we have obtained a low-entropy symbolic expression which is far superior to the one given in Eq. (1.6)

The EET, quite naturally, also allows for the value of a dependent source to become infinite so that a particular transfer becomes simplified in the same manner as that of an ideal operational amplifier circuit. In the case of  $R_{in}$  in Fig. 1.3, the EET allows us to write:

$$R_{in} = R_{in}|_{g_m \rightarrow \infty} \frac{1 + \frac{1}{g_m \bar{\mathcal{G}}^{(m)}}}{1 + \frac{1}{g_m \bar{\mathcal{G}}^{(m)}}} \quad (1.13)$$

in which  $\bar{\mathcal{G}}^{(m)}$  and  $\bar{\mathcal{G}}^{(m)}$  are the same as before and  $R_{in}|_{g_m \rightarrow \infty}$  is determined in Fig. 1.5. The gain from  $v_1$  to  $g_m v_1$  reminds us of an opamp connected in some kind of

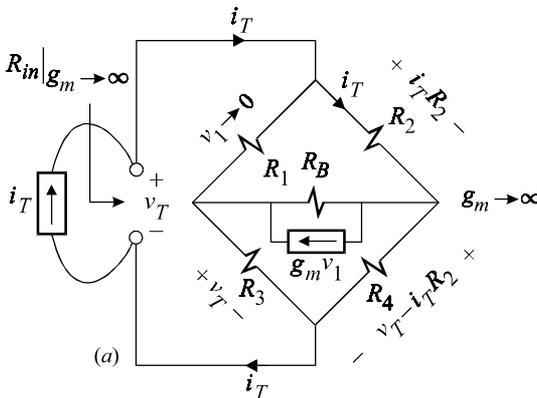


Figure 1.5

feedback fashion whose details we do not need to know at all. Now, if we let  $g_m$  become infinite, then  $v_1 \rightarrow 0$  very much in the same manner as the differential input voltage of an opamp tends to zero when the gain becomes infinite and the output voltage stays finite. We can see in Fig. 1.5 that, with  $g_m \rightarrow \infty$  and  $v_1 \rightarrow 0$ , the current through  $R_1$  becomes zero and  $i_T$  flows entirely through  $R_2$  creating a voltage drop  $i_T R_2$  across it. At the same time,  $v_T$  appears across  $R_3$  causing a current  $v_T/R_3$  to flow through it. We can also see that the voltage drop across  $R_4$ , when  $v_1 = 0$ , is equal to  $v_T - i_T R_2$  so that the current through it is simply  $(v_T - i_T R_2)/R_4$ . Summing the currents at the lower node of the bridge, we obtain:

$$i_T = \frac{v_T}{R_3} + \frac{v_T - i_T R_2}{R_4} \quad (1.14)$$

It follows from Eq. (1.14) that:

$$\frac{v_T}{i_T} = R_{in} |_{g_m \rightarrow \infty} = \frac{R_3 \parallel R_4}{1 + \frac{R_2}{R_4}} \tag{1.15}$$

Substituting Eq. (1.15) in (1.13) we obtain another expression for  $R_{in}$  given by:

$$R_{in} = \frac{R_3 \parallel R_4}{1 + \frac{R_2}{R_4}} \frac{1 + \frac{1 + R_2 \parallel R_4 / R_B}{g_m(R_B + R_2 \parallel R_4) \parallel R_1 \parallel R_3}}{1 + \frac{1 + R_2 / R_1}{g_m(R_1 + R_2) \parallel R_B \parallel (R_3 + R_4)}} \tag{1.16}$$

Although Eq. (1.16) looks simpler than Eq. (1.12), both are very useful analytical expressions. For very small values of  $g_m$ , Eq. (1.12) is a better expression because the bilinear factor containing  $g_m$  is close to unity and  $R_{in}$  is mostly dictated by the bridge circuit. If on the other hand  $g_m$  is very large, Eq. (1.16) is a better expression because  $R_{in}$  is mostly given by Eq. (1.15), and the bilinear function of  $g_m$  in Eq. (1.16) is close to unity.

### 1.4 Input impedance of a reactive bridge circuit with a dependent source

Consider now the reactive bridge circuit in Fig. 1.6 for which the input impedance<sup>2</sup> is to be determined. By designating the capacitor as the extra element, we will show how easily  $Z_{in}(s)$  can be determined by simply analyzing a few purely resistive

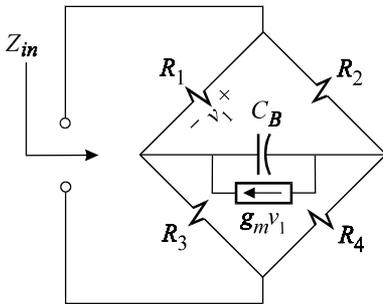


Figure 1.6

circuits. In other words, we will see how the EET allows one to determine a reactive transfer function, such as  $Z_{in}(s)$ , without ever having to deal with a reactive component such as  $1/sC_B$ . In fact, as we will see later, the most natural application of the EET and NEET is in the reduction of a circuit with  $N$  reactive elements to a set of purely resistive circuits.

If we designate  $Z_B = 1/sC_B$  as the extra element and let  $Z_B \rightarrow \infty$ , we obtain the

circuit in Fig. 1.7a, which is a special case of the circuit in Fig. 1.3 whose input impedance is given by Eq. (1.12). The derivation of the input impedance of the circuits in Figs. 1.3 and 1.7a are identical, with the exception that  $R_B \rightarrow \infty$  in Fig. 1.7a. Hence, by letting  $R_B \rightarrow \infty$  in Eq. (1.12) we obtain for Fig. 1.7a:

$$Z_{in}(s)|_{Z_B \rightarrow \infty} = (R_1 + R_3) \parallel (R_2 + R_4) \frac{1 + g_m R_1 \parallel R_3}{1 + \frac{g_m R_1}{1 + (R_1 + R_2)/(R_3 + R_4)}} \quad (1.17)$$

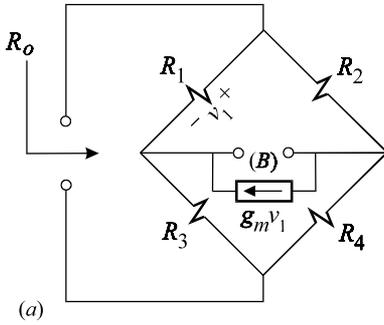


Figure 1.7

To obtain  $Z_{in}(s)$ , all we need to do is determine  $\mathcal{R}^{(B)}$  and  $R^{(B)}$ , shown in Figs. 1.7b and c, respectively, and apply the EET:

$$\begin{aligned} Z_{in}(s) &= Z_{in}(s)|_{Z_B \rightarrow \infty} \frac{1 + \frac{\mathcal{R}^{(B)}}{Z_B}}{1 + \frac{R^{(B)}}{Z_B}} \\ &= R_o \frac{1 + sC_B \mathcal{R}^{(B)}}{1 + sC_B R^{(B)}} \end{aligned} \quad (1.18)$$

in which  $R_o = Z_{in}(s)|_{Z_B \rightarrow \infty}$  and is given by Eq. (1.17).

In Fig. 1.7b, the current  $i_T$  is given by the sum of  $g_m v_1$  and the current through the branch  $R_1 \parallel R_3 + R_2 \parallel R_4$ , so that we have:

$$i_T = g_m v_1 + \frac{v_T}{R_1 \parallel R_3 + R_2 \parallel R_4} \quad (1.19)$$

In Fig. 1.7b we can also see that:

$$v_1 = v_T \frac{R_1 \parallel R_3}{R_1 \parallel R_3 + R_2 \parallel R_4} \quad (1.20)$$

Substituting Eq. (1.20) in (1.19), we obtain:

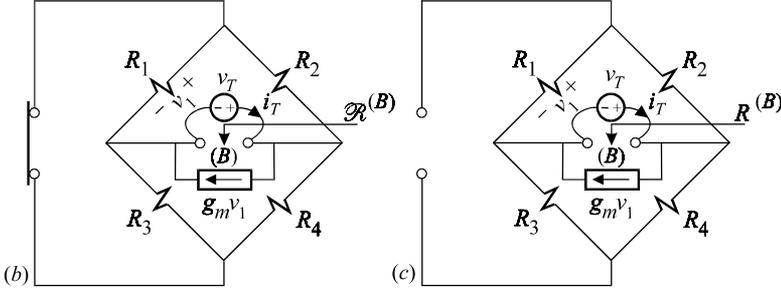


Figure 1.7 (cont.)

$$\mathcal{R}^{(B)} = \frac{v_T}{i_T} = \frac{R_1 \parallel R_3 + R_2 \parallel R_4}{1 + g_m R_1 \parallel R_3} \quad (1.21)$$

In Fig. 1.7c, the current  $i_T$  consists of the sum of  $g_m v_1$  and the current through the branches  $(R_1 + R_2)$  and  $(R_3 + R_4)$  so that we have:

$$i_T = g_m v_1 + \frac{v_T}{R_1 + R_2} + \frac{v_T}{R_3 + R_4} \quad (1.22)$$

In Fig. 1.7c we can also see that:

$$v_1 = v_T \frac{R_1}{R_1 + R_2} \quad (1.23)$$

Substituting Eq. (1.23) in (1.22) we obtain:

$$i_T = \frac{v_T(g_m R_1 + 1)}{R_1 + R_2} + \frac{v_T}{R_3 + R_4} \quad (1.24)$$

whence it follows that:

$$R^{(B)} = \frac{v_T}{i_T} = \frac{R_1 + R_2}{1 + g_m R_1} \parallel (R_3 + R_4) \quad (1.25)$$

With  $\mathcal{R}^{(B)}$  and  $R^{(B)}$  determined, we can write  $Z_{in}(s)$  in Eq. (1.18) in pole-zero form:

$$Z_{in}(s) = R_o \frac{1 + s/\omega_z}{1 + s/\omega_p} \quad (1.26)$$

in which:

$$\omega_z = \frac{1}{C_B \mathcal{R}^{(B)}} = \frac{1 + g_m R_1 \parallel R_3}{C_B (R_1 \parallel R_3 + R_2 \parallel R_4)} \quad (1.27)$$

$$\omega_p = \frac{1}{C_B R^{(B)}} = \frac{1}{C_B \frac{R_1 + R_2}{1 + g_m R_1} \parallel (R_3 + R_4)} \quad (1.28)$$

And such are the joys of network analysis!

## 1.5 Review

Although the matrix algebra of nodal or loop analysis is useful in obtaining numerical solutions of linear electrical circuits, it is not useful in obtaining *meaningful* analytical results in symbolic form. An analytical answer is not a mere collection of symbols but an answer in which the symbols are arranged in useful, or low-entropy, forms such as series-parallel combinations and ratios of various elements and time constants. This book presents efficient analytical tools for fast derivation of low-entropy results for electrical circuits. One such analytical tool is the extra element theorem (EET) which we have introduced in this chapter by way of examples in which the input impedance of various bridge circuits is determined.

## Problems

**1.1 High entropy versus low entropy.** In order to appreciate the difference between high- and low-entropy expressions, consider the following for the input impedance of the circuit in the black box:

$$R_{in} = \frac{R_4 R_1 R_2 + R_4 R_1 R_3 + R_4 R_2 R_3}{R_4 R_2 + R_3 R_4 + R_1 R_2 + R_1 R_3 + R_2 R_3} \quad (1.29)$$

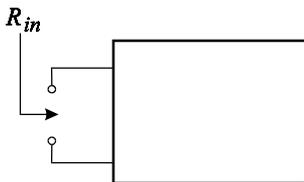


Figure 1.8

Are you able to make anything out of this expression? How does this expression simplify if  $R_2 \ll R_3$ ? Consider now:

$$R_{in} = R_4 \parallel (R_1 + R_2 \parallel R_3) \quad (1.30)$$

Show that the two expressions above are equivalent. Which of the two is more

meaningful? Using Eq. (1.30) show that when  $R_2 \ll R_3$ , we have the following simplification:

$$R_{in} \approx R_4 \parallel (R_1 + R_2) \tag{1.31}$$

**1.2 Impedance using the EET.** Following the example in Section 1.2, show in a few steps that the input impedance of the circuit below is given by:

$$Z_{in} = R_o \frac{1 + s/\omega_1}{1 + s/\omega_2} \tag{1.32}$$

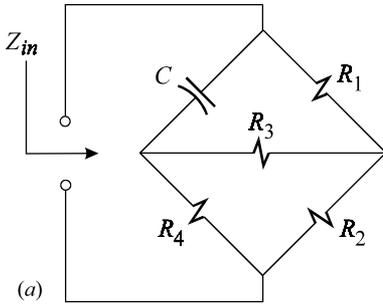


Figure 1.9

where:

$$\left. \begin{aligned} R_o &= R_1 + R_2 \parallel (R_3 + R_4) \\ \omega_1 &= \frac{1}{CR_4 \parallel (R_3 + R_1 \parallel R_2)} \\ \omega_2 &= \frac{1}{C[R_1 + R_3 \parallel (R_4 + R_2)]} \end{aligned} \right\} \tag{1.33a, b, c}$$

*Hint:* Refer to Figs. 1.9b, c and d below and apply the EET in Eq. (1.4).

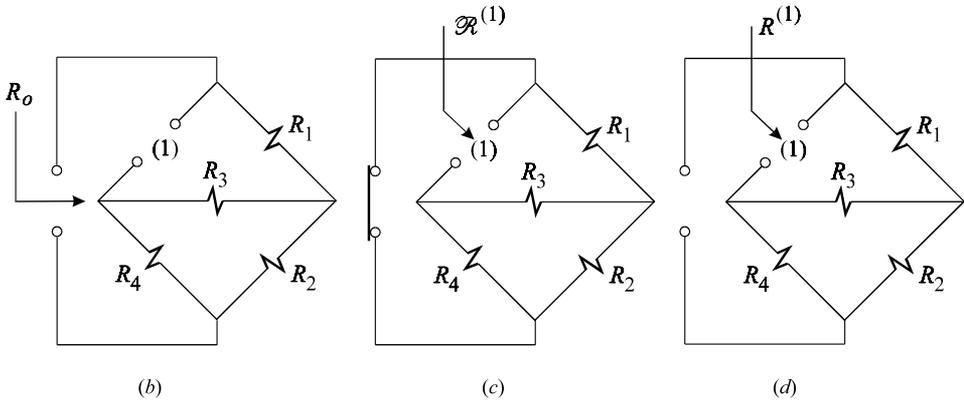


Figure 1.9 (cont.)

**1.3 Output resistance of a current source using the EET.** Show that the output resistance of the BJT current source in Fig. 1.10a, using the equivalent circuit model in Fig. 1.10b, is given by:

$$R_{out} = \frac{r_\mu + R_s}{1 + \frac{R_s}{R_E}} \frac{1 + \frac{1}{g_m r_\pi} \left( 1 + \frac{r_\pi + R_s \parallel r_\mu}{R_E \parallel r_o} \right)}{1 + \frac{1}{g_m r_o} \left[ 1 + \frac{r_\mu + r_o}{r_\pi \parallel (R_s + R_E)} \right]} \quad (1.34)$$

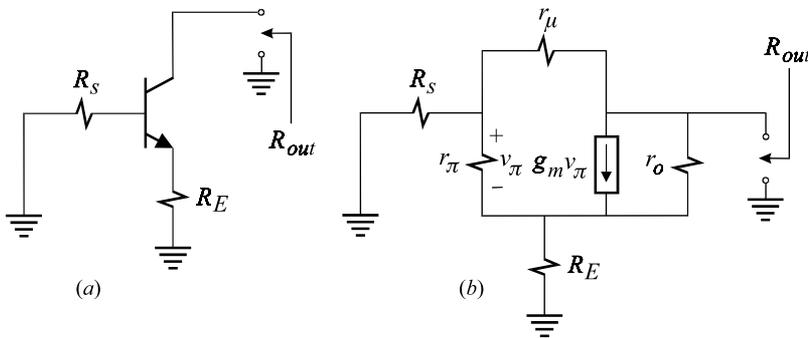


Figure 1.10

Hint: Refer to the example in Section 1.3 and to Figs. 1.10c–e below.

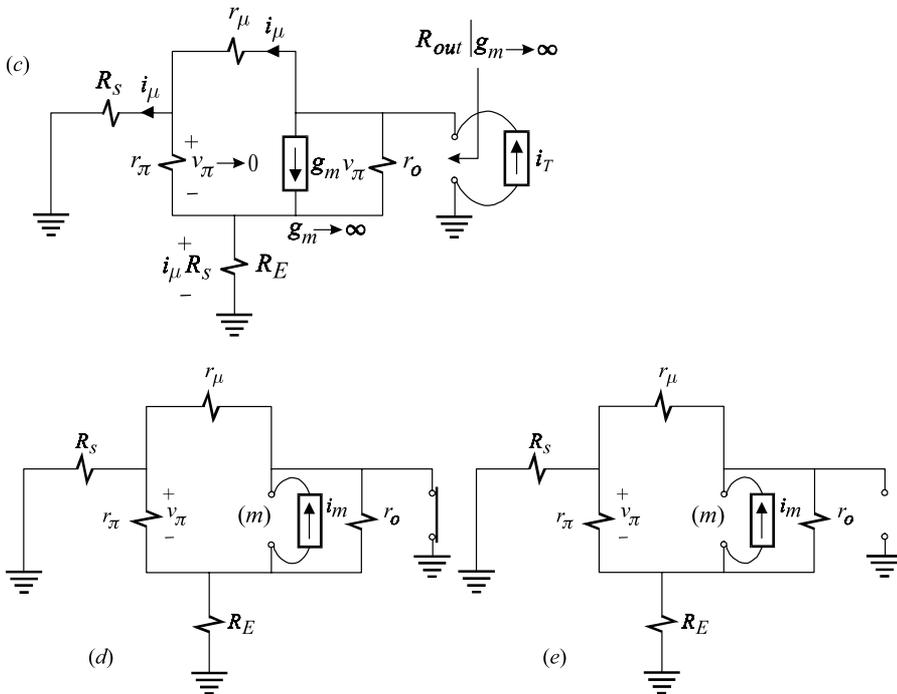


Figure 1.10 (cont.)

## REFERENCES

---

1. R. D. Middlebrook, “Low-entropy expressions: the key to design-oriented analysis”, *IEEE Frontiers in Education, Twenty-First Annual Conference*, Purdue University, Sept. 21–24, 1991, pp. 399–403.
2. V. Vorpérian, “Improved circuit analysis techniques require minimum algebra”, *Electronic Design News*, August 3, 1995, pp. 125–134.
3. R. D. Middlebrook, “Null double injection and the extra element theorem”, *IEEE Transactions on Education*, Vol. 32, No. 3, August 1989, pp. 167–180.
4. R. D. Middlebrook, V. Vorpérian, J. Lindal, “The  $N$  Extra Element Theorem”, *IEEE Transactions on Circuits and Systems – I: Fundamental Theory and Applications*, Vol. 45, No. 9, Sept. 1998, pp. 919–935.
5. L. O. Chua and Pen-Min Lin, *Computer Aided Analysis of Electronic Circuits: Algorithms and Computational Techniques*, Prentice Hall, New York, 1975, pp. 568–569.